

3.)

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 = 450 \Omega \pm 2\%$$

$$R_2 = 750 \Omega \pm 1\%$$

$$R = 112,5 \Omega$$

$$f_{R_1} = \frac{R_2}{R_1 + R_2} - \frac{R_1 R_2}{(R_1 + R_2)^2}$$

$$f_{R_2} = \frac{R_1}{R_1 + R_2} - \frac{R_1 R_2}{(R_1 + R_2)^2}$$

$$dR = \left[\frac{R_2}{R_1 + R_2} - \frac{R_1 R_2}{(R_1 + R_2)^2} \right] dR_1 + \left[\frac{R_1}{R_1 + R_2} - \frac{R_1 R_2}{(R_1 + R_2)^2} \right] dR_2$$

$$dR = (0,0625 \cdot 2) + (0,5625 \cdot 1)$$

$$\underline{dR = 0,6875 \Omega}$$

$$\underline{dR = 0,0067}$$

$$\delta R = \frac{0,6875 \Omega}{112,5 \Omega} \cdot 100\% \approx 0,61\%$$