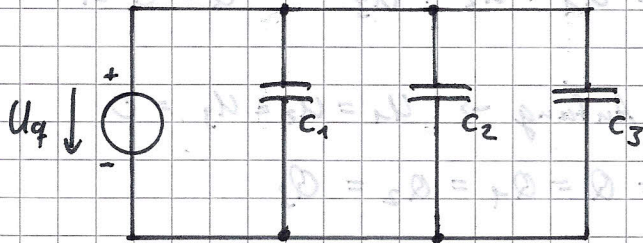


## Parallelschaltung von Kondensatoren




$$U_q = U_1 = U_2 = U_3$$

$$Q = Q_1 + Q_2 + Q_3$$

$$C_{ges} \cdot U_q = C_1 U_1 + C_2 U_2 + C_3 U_3 \quad | \quad U_q = U_1 = U_2 = U_3$$

$$C_{ges} = C_1 + C_2 + C_3$$

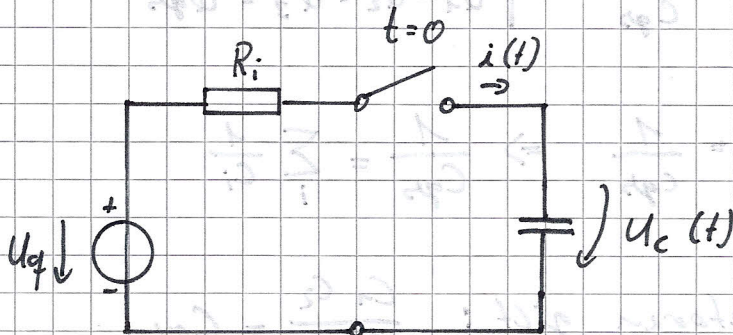

$$U_c(t=0) = 0 \quad q(t=0) = 0$$

$$U_q = U_R + U_c \rightarrow U_q = i \cdot R_i + U_c$$

$$q = C \cdot u$$

$$t = 0 : U_c = 0 \rightarrow U_q = i R_i \rightarrow i(t=0) = \frac{U_q}{R_i}$$

$$i = \frac{dq}{dt} = i_v = \frac{d\varphi}{dt}$$

↑  
Verschiebungsstrom im Dielektrikum

$$i = \frac{d\varphi}{dt} = \frac{dq}{dt} \rightarrow dq = d(u \cdot C)$$

$$i = \frac{d(C \cdot u)}{dt} = \frac{C \cdot du}{dt} + \frac{u \cdot dC}{dt} \rightarrow \frac{dC}{dt} = 0 \rightarrow \text{const}$$