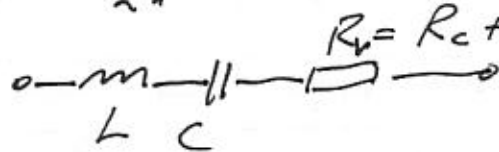


# HF 1. Übung / Lösungen

$$1. a) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-5} \cdot 10^{-8}}} \text{ s}^{-1} = 10^7 \text{ s}^{-1}$$

$$f_0 = \frac{\omega_0}{2\pi} = 1,59155 \text{ MHz}$$



$$R_V = R_C + R_L$$

$$R_L = \tan \delta_L \cdot \omega_0 L$$


$$R_C = \tan \delta_C \cdot \frac{1}{\omega_0 C}$$

$$\omega_0 L = \frac{1}{\omega_0 C} = Z_0 = 100 \Omega$$

$$R_V = (1 + 0,2) \cdot 10^{-2} \cdot 100 \Omega = 1,2 \Omega$$

$$\rightarrow Q = \frac{Z_0}{R_V} = \frac{100 \Omega}{1,2 \Omega} = 83 \frac{1}{3}$$

$$B = \frac{f_0}{Q} = 19,1 \text{ kHz}$$

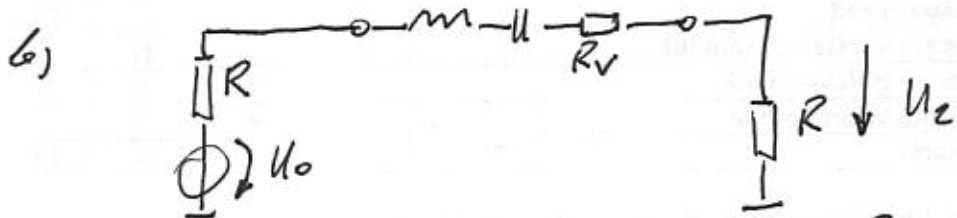

$$Q_B = \frac{Z_0}{R_V + 2R} = 10 \rightarrow R_V + 2R = \frac{Z_0}{10}$$

$$\underline{R = 4,4 \Omega}$$


bei  $f = f_0$  und  $R_V = 0$  gilt  $U_2 = \frac{U_0}{2}$

" " "  $R_V = 1,2 \Omega$  "  $U_2 = U_0 \cdot \frac{R}{2R + R_V}$

$$\rightarrow a_0 / \text{dB} = 20 \lg \left\{ \frac{\frac{U_0}{2}}{U_0 \cdot \frac{R}{2R + R_V}} \right\}$$

$$= 20 \lg \left\{ \frac{2R + R_V}{2R} \right\} = 1,11 \text{ dB}$$

2. a)

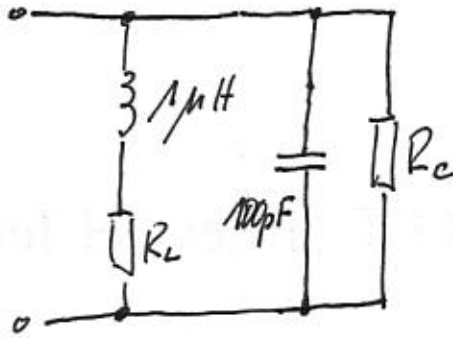

$$\omega_0 \approx 10^8 \text{ s}^{-1}, Z_0 = 100 \Omega$$


$$Y_0 = 10 \text{ mS}$$

$$R_c = \frac{1}{Y_0 \cdot \tan \delta_c} = 20 \text{ k}\Omega$$

$$R_L = 100 \Omega \cdot \tan \delta_L = 2 \Omega$$

$$f_0 \approx \frac{1}{2\pi \sqrt{LC}} = 15,9155 \text{ MHz}$$

Ersatzsystem

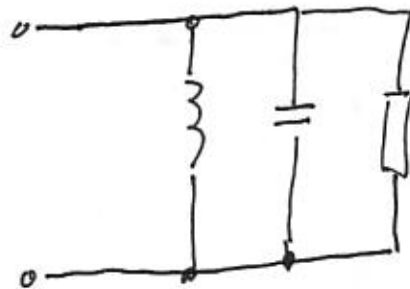


$$R_p = R_c \parallel R_L(1+Q_L^2) = 20 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 4 \text{ k}\Omega$$

b)

$$L = \frac{n^2}{R_m} \rightarrow n^2 = L \cdot R_m = 10^{-6} \text{ H} \cdot 2,5 \cdot 10^9 \text{ H} = 2500$$

$$n = 50$$

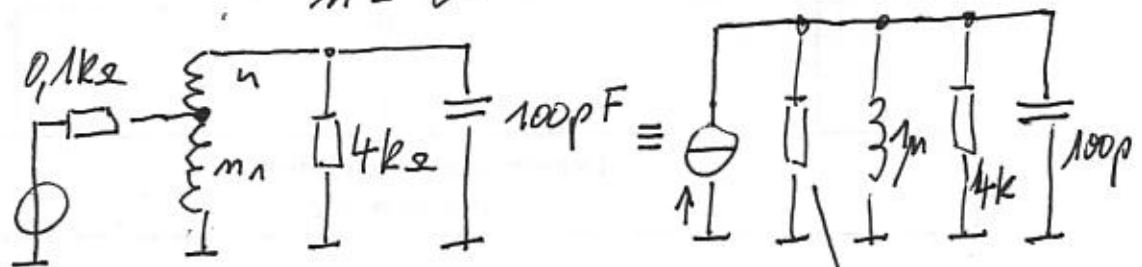

$$\frac{U_0}{1 \text{ k}\Omega} \cdot \frac{n_1}{n} \quad 0,1 \text{ k}\Omega \cdot \left(\frac{n}{n_1}\right)^2$$


$$B = 1,5 \text{ MHz} \rightarrow Q_B = \frac{f_0}{B} = 10,61 = \frac{(4 \text{ k}\Omega \parallel 0,1 \text{ k}\Omega \cdot \frac{n^2}{n_1^2})}{100 \Omega}$$

$$\rightarrow 0,1 \text{ k}\Omega \cdot \frac{n^2}{n_1^2} = 1,444 \text{ k}\Omega \rightarrow n_1 = 13,16 \text{ Wdg.}$$

$n_1 = 13$  Wdg gewählt.

# HF 1. Übung (Lösungen)

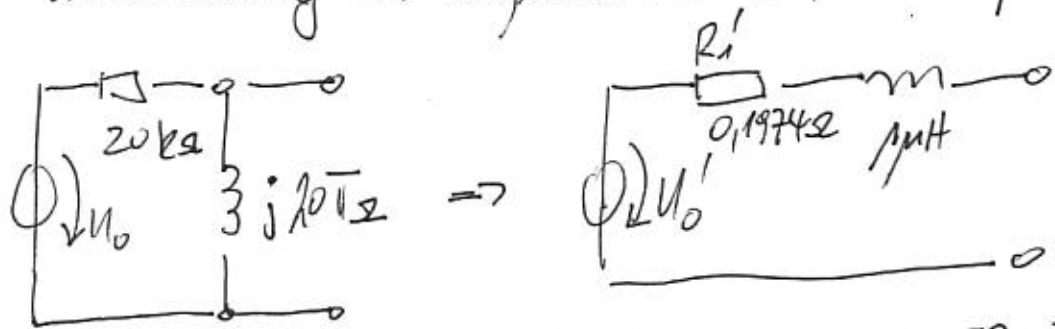
3. Umrechnung in äquivalente RS bei  $f_0$



$$Z_i = j \frac{20 \cdot 10^3 \cdot 20 \pi \Omega^2}{20 \cdot 10^3 \Omega + j 20 \pi \Omega} = \frac{(20 \text{ k}\Omega - j 20 \pi \Omega) j 4 \cdot 10^5 \Omega^2}{(20 \text{ k}\Omega)^2 + (20 \pi \Omega)^2}$$

$$\approx \frac{(20 \text{ k}\Omega - j 20 \pi \Omega) \cdot j 20 \pi}{20 \cdot 10^3}$$
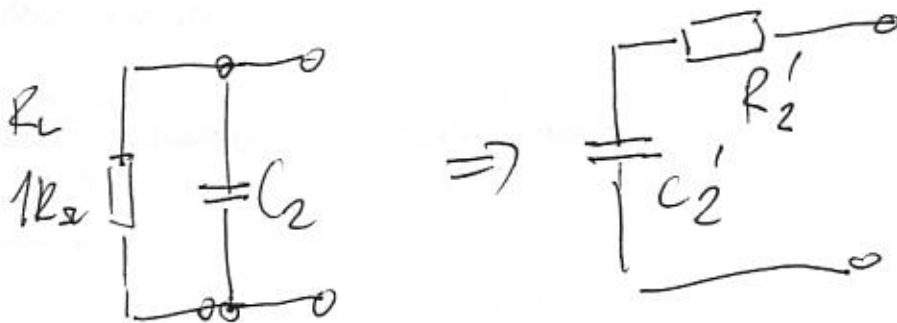
$$= j 20 \pi \Omega + \frac{20 \pi^2}{1000} \Omega \approx j 20 \pi \cdot 1 \mu\text{H} + \underline{0,1974 \Omega}$$



mit  $Q_B = \frac{10 \text{ MHz}}{0,2 \text{ MHz}} = 50$  und  $Z_0 = \omega_0 L = 20 \pi \Omega$

$$\rightarrow R_1' + R_2' = \frac{Z_0}{Q_B} = 1,2566 \Omega$$

$$\rightarrow R_2' = (1,2566 - 0,1974) \Omega = \underline{1,0592 \Omega}$$

bei  $f_0$

$$Z_2 = \frac{R_L}{1 + j \omega_0 R_L C_2} = \frac{R_L (1 - j \omega_0 R_L C_2)}{1 + (\omega_0 R_L C_2)^2}$$

# HF 1. Übung / Lösungen

weiter zu 3.

$$R_2' = \frac{R_L}{1 + (\omega_0 R_L C_2)^2} = 1.0592 \Omega$$

$$\rightarrow (\omega_0 R_L C_2)^2 = \frac{1k\Omega}{1.0592\Omega} - 1 = 943.0757$$

$$\omega_0 R_L C_2 = 30.7095 \rightarrow C_2 = 488.76 \text{ pF}$$

$$\text{Im}\{Z_2\} = -\frac{(\omega_0 R_L C_2) R_L}{1 + (\omega_0 R_L C_2)^2} = -32.5287 \Omega$$

$$\rightarrow X_{C1} = \frac{1}{\omega C_1} = Z_0 - 32.5287 \Omega = 30.3032 \Omega$$

$$\rightarrow C_1 = 525.21 \text{ pF}$$