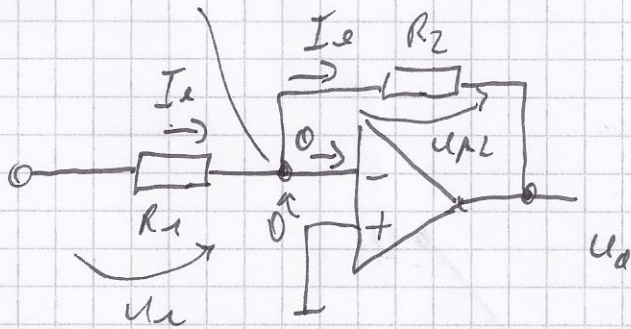


Integrierte Strukturschicht


virtuelle Masse

(IST
VL 2012)



$$I_e = \frac{U_e}{R_1} \quad U_{pr2} = U_e \cdot \frac{R_2}{R_1}$$
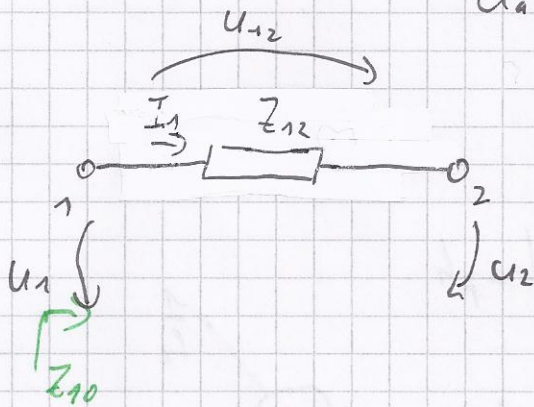
$$U_a = -U_{pr2} = -U_e \cdot \frac{R_2}{R_1}$$





$$v_u = U_2 = U_1$$

$$I_1 = \frac{U_1 - v_u U_1}{Z_{12}}$$

$$= \frac{U_1}{Z_{12}} (1 - v_u)$$

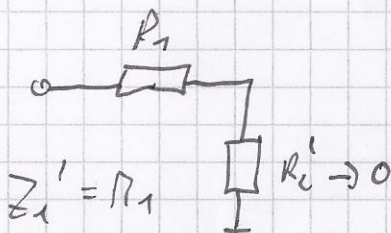
$$Z_{10} = \frac{U_1}{I_1} = \frac{Z_{12}}{1 - v_u}$$





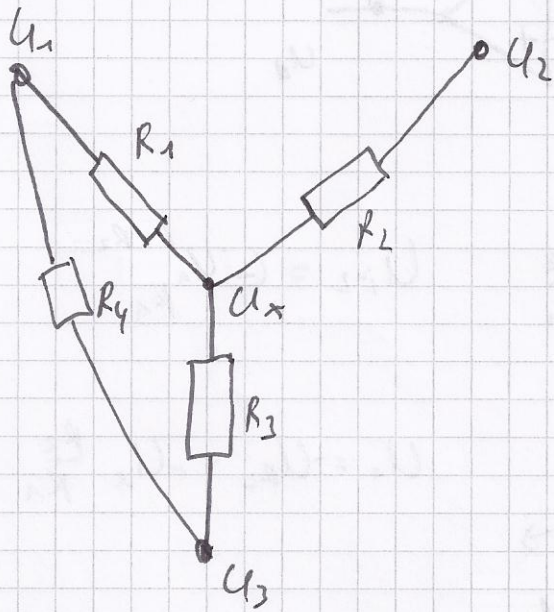

⇓

Masaru-graph

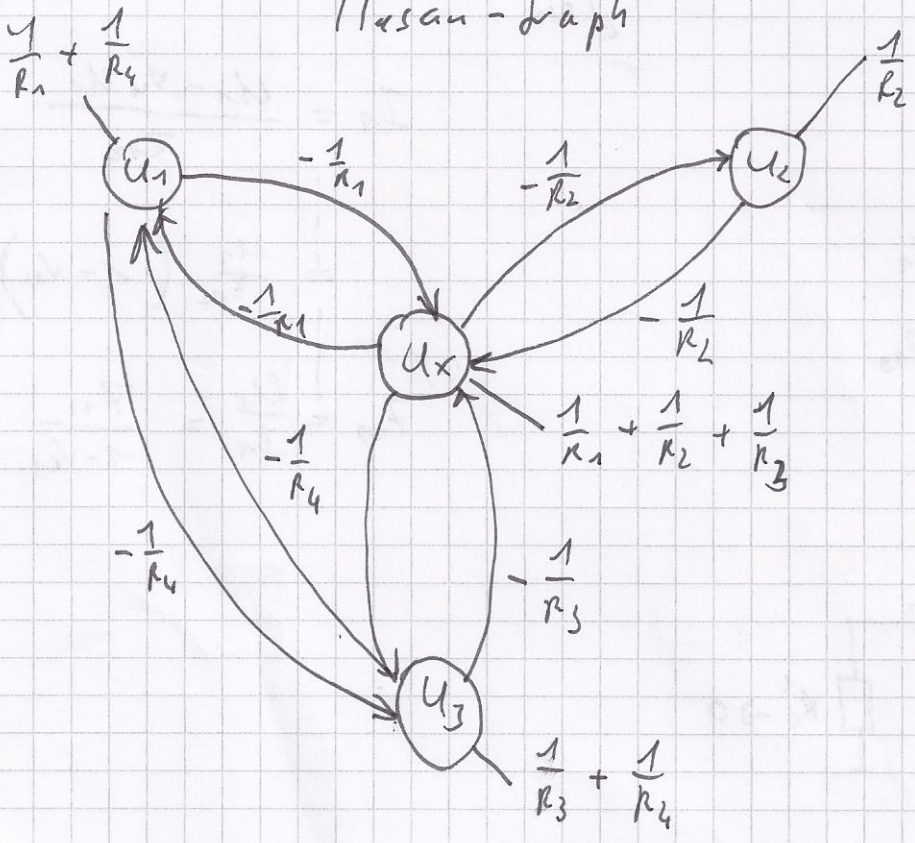

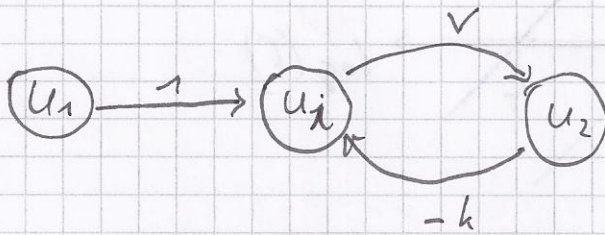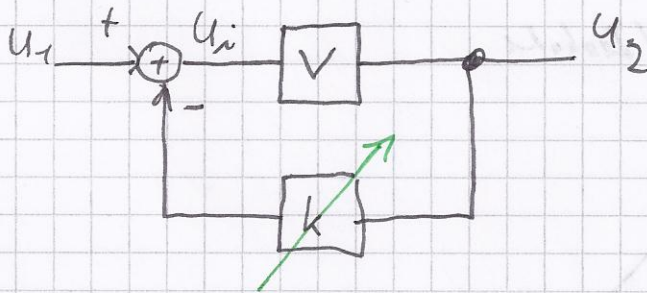

$$U_2 = U_1 \cdot v + U_2 \cdot (-k) \cdot v$$

$$U_2 (1 + kv) = U_i \cdot v$$

$$v' = \frac{U_2}{U_1} = \frac{v}{1 + kv} = \frac{v}{g}$$

$v' \rightarrow$ Verstärkung des rückgekoppelten System

$g = 1 + kv \rightarrow$ Rückkopplungsgrad



Bei $kv = -1$ geht v' gegen unendlich und das System ist nicht stabil.

$$|kv| = 1$$

$$P_{kv} = 180^\circ + n \cdot 360^\circ$$

$$\text{Phasenrand } \varphi_R = 180^\circ + \varphi_{f_1}$$

1. Übungsaufgabe

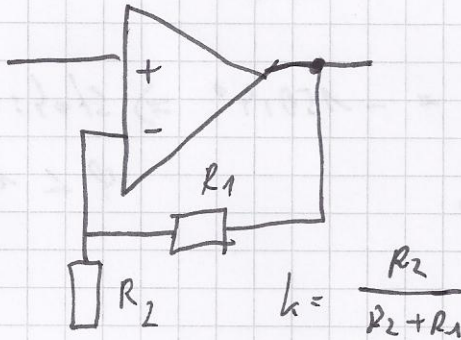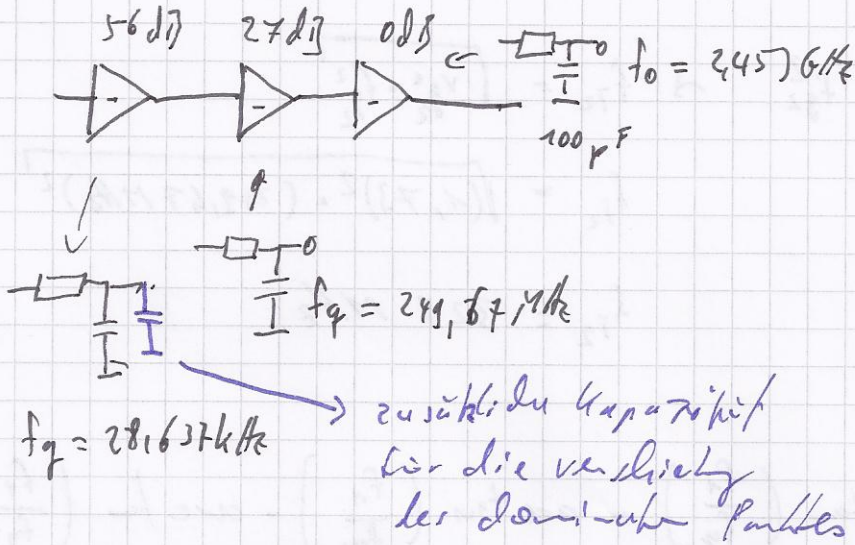


$$V = \frac{V_1}{1 + j \frac{f}{f_{q1}}} \cdot \frac{V_2}{1 + j \frac{f}{f_{q2}}} \cdot \frac{V_3}{1 + j \frac{f}{f_{q3}}}$$

$$V_0 = V_1 + V_2 + V_3 = 83,6 \text{ dB} = 15100$$

$$f_T = 15100 \cdot f_0 = 432 \text{ MHz}$$

$$v_{q2} = \frac{f_T}{f_{q2}} = 1,73$$

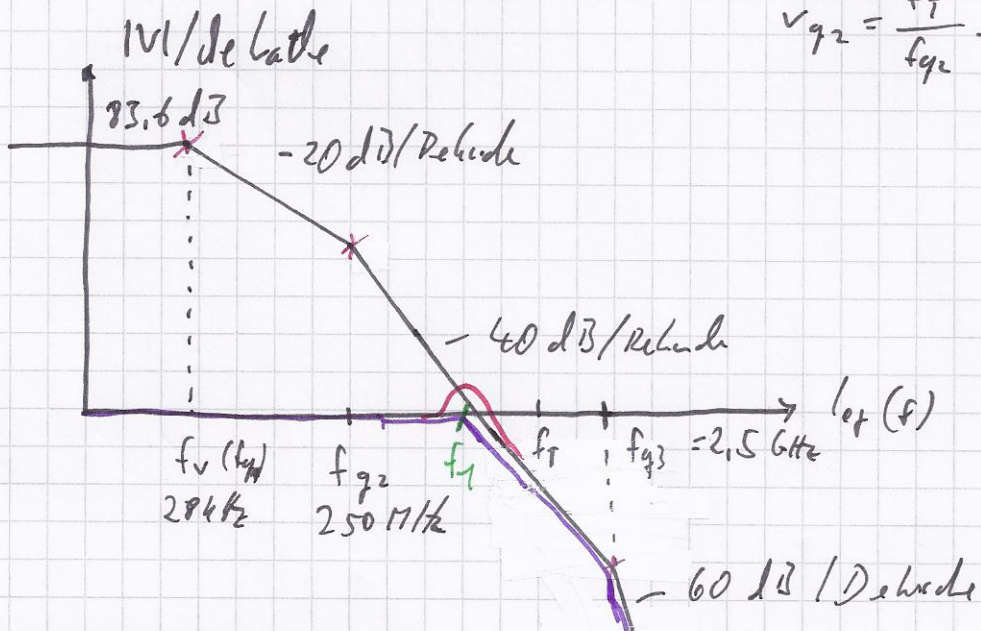

Transitfrequenz 2. Ordnung

1.

$$f_{T2}^2 = v_{g2} \cdot f_{g2}^2 \quad \rightarrow \quad f_{T2} = \sqrt{v_{g2}^2 \cdot f_{g2}^2}$$

$$f_{T2} = \sqrt{(1,73)^2 \cdot (249,67 \text{ MHz})^2}$$

$$f_{T2} = 328 \text{ MHz}$$

2.

$$\varphi = -\arctan\left(\frac{f_1}{f_{g1}}\right) - \arctan\left(\frac{f_1}{f_{g2}}\right) - \arctan\left(\frac{f_1}{f_{g3}}\right)$$

$$\varphi \approx -90^\circ - 52,8^\circ - 7,6^\circ = -150,4^\circ \Rightarrow \text{stabil da}$$

$$\varphi_R = 29,6^\circ = 180^\circ + \varphi \quad \varphi < 180^\circ$$

7.


$$\varphi_R = 60^\circ = 180 + \varphi$$

$$60^\circ - 180^\circ = \varphi = -120^\circ$$

$$\text{für } \varphi_R = 60^\circ \leadsto f_1 \leq 127 \text{ MHz}$$

$$v' = \frac{f_T}{f_1} = 3,33 \approx 3,4$$

Vertiefung des dominanten Poles

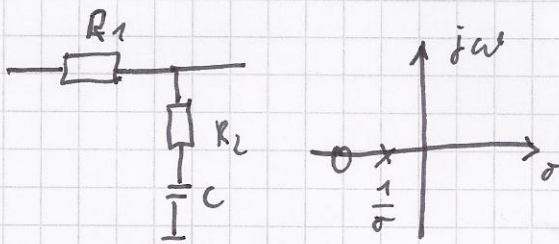

$$\frac{1 + j\omega R_2 C}{1 + j\omega (R_1 + R_2) C}$$



- Polnullstelle - Kompensation
- pole - Splitting
- Miller - Kompensation